

1. What are the states for the circuit controlling the steering?

The states of the circuit represent the steering wheel position, which can be Left and Right. These two states indicate the current position of the steering wheel.


2. What are the inputs to the circuit and what values can those inputs have?

The inputs to the circuit are the car's position within the lane, which can have three values: Middle of a lane, Drifting to the right edge of the lane, and Drifting to the left edge of the lane.

3. Draw the finite state table and finite state diagram for this circuit.

Finite State Table:

Current State	Input = Middle	Input = Driving to Right	Input = Driving to Left
Left	Left	Left	Right
Right	Right	Left	Right

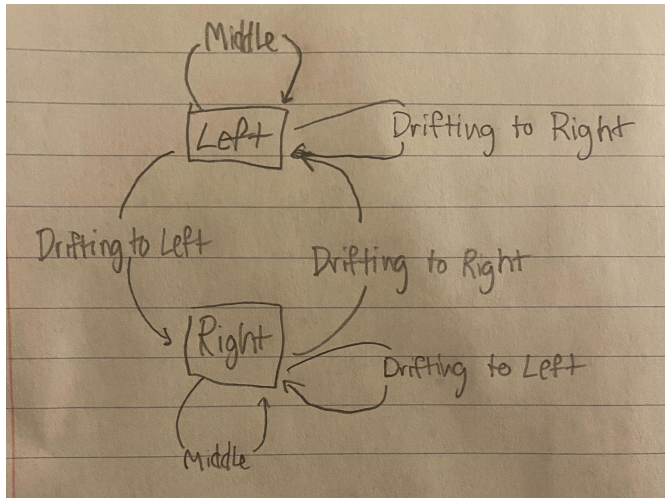

1. What are the states for the circuit controlling the walkway?

The states of the circuit represent the motion direction of the walkway, which can be: Off, Moving Northward, and Moving Southward. These three states indicate the current operational state of the walkway.

2. What are the inputs to the circuit and what values can those inputs have?

The inputs to the circuit are the readings from the two weight sensors: North sensor (N): Can be 0 (no weight) or 1 (weight detected) and South sensor (S): Can be 0 (no weight) or 1 (weight detected)

This gives us four possible input combinations: (N=0, S=0): No weight on either sensor, (N=0, S=1): Weight on South sensor only, (N=1, S=0): Weight on North sensor only, and (N=1, S=1): Weight on both sensors

3. Draw the finite state table and finite state diagram for this circuit.

Finite State Table:

Current State	Input (N,S) = (0,0)	Input (N,S) = (0,1)	Input (N,S) = (1,0)	Input (N,S) = (1,1)
Off	Off	Northward	Southward	Off
Northward	Off	Northward	Northward	Northward
Southward	Off	Southward	Southward	Southward

